
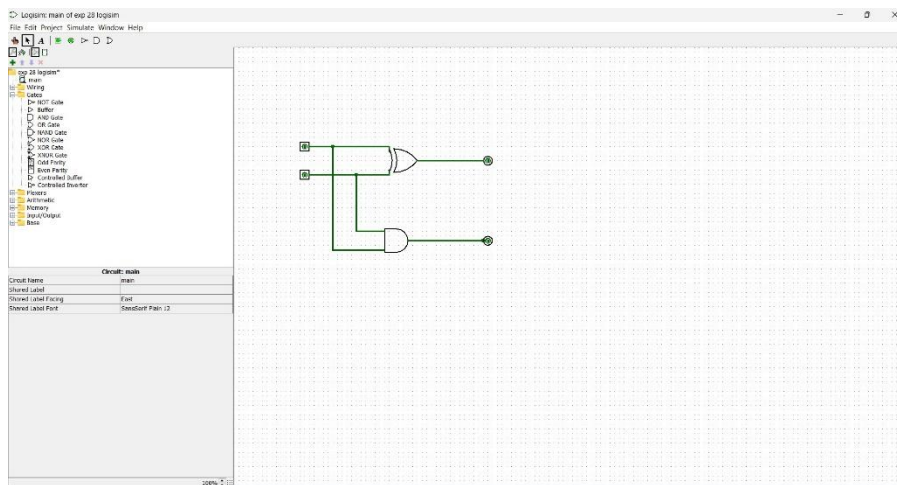


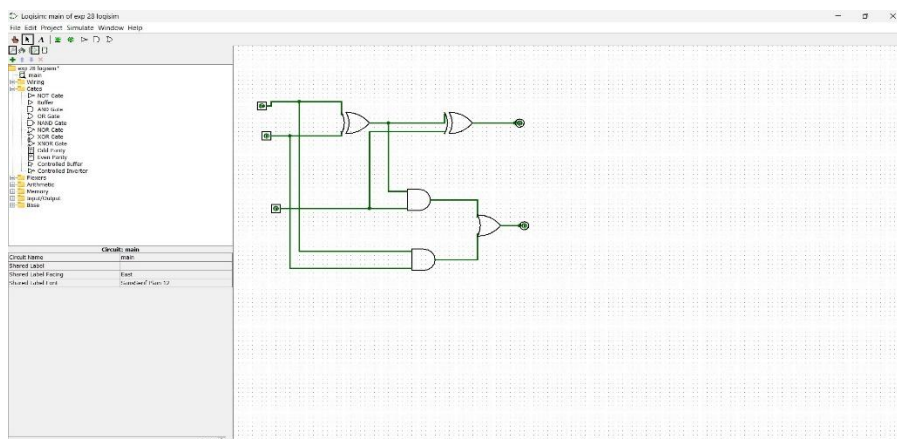
Design a circuit for the below mentioned diagram and implement the same using Logisim simulator.




Design a circuit for the below mentioned diagram and implement it using Logisim simulator.




Half adder using nand gate

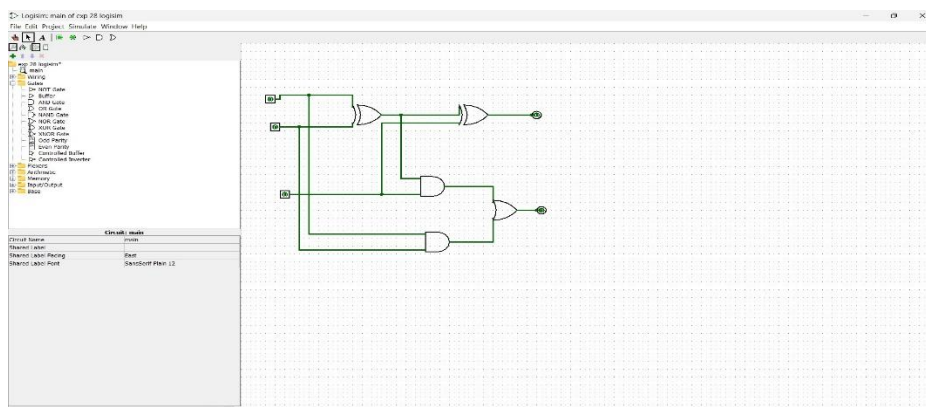

Half adder using nor gate

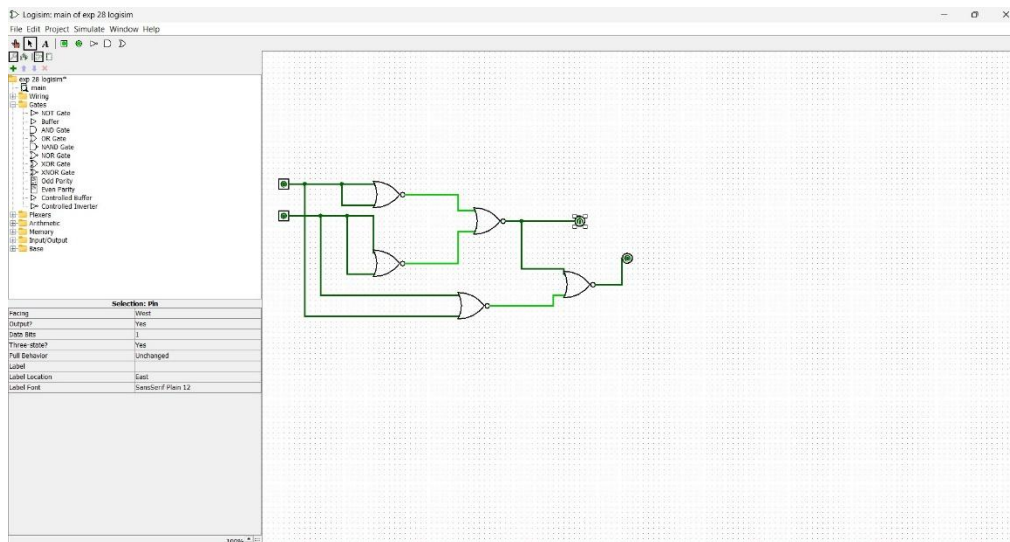

Full adder using nand gate

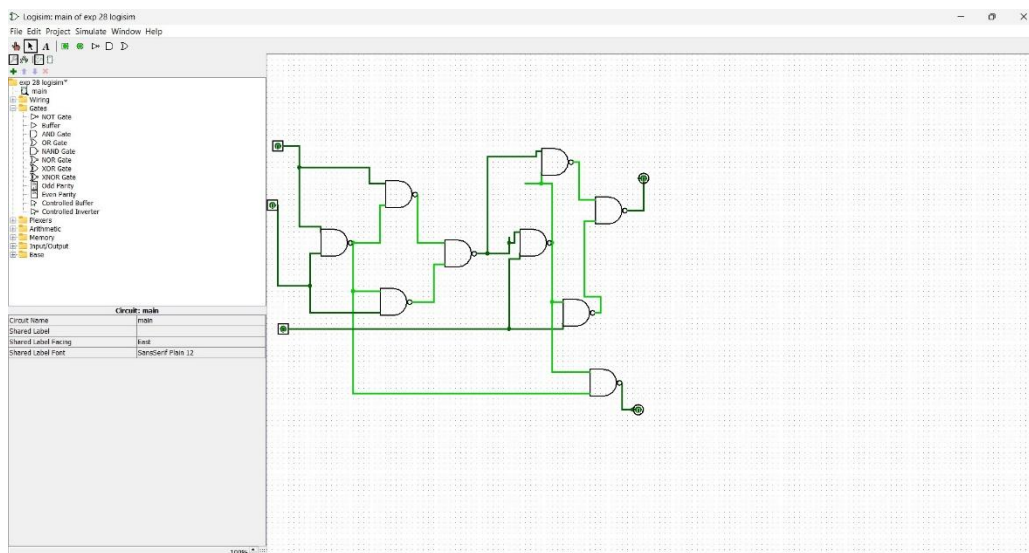

Full adder (or)gate

